
Computer Organization Lab 2

0113110 Po-Han Chen, 0316213 Yu-Wen Pwu

Architecture Diagram

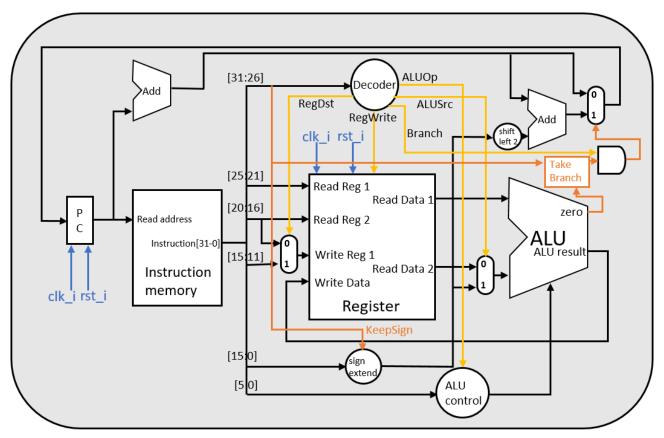

Top module: Simple_Single_CPU

Detailed Description of the Implementation

- ALU Operations
 - 0: src1_i & src2_i
 - o 1: src1_i | src2_i
 - o 2: src1_i + src2_i
 - 6: src1_i src2_i
 - o 7: src1_i < src2_i</p>
 - o 12: ~(src1_i | src2_i)
 - 14: src2_i_signed >>> src1_i_signed
 - o 15: src2_i << 16

- ALU Control (input [5:0] funct_i)
 Case (funct_i)
 - o 3: ALUCtrl o = 14; // SRA
 - o 7: ALUCtrl_o = 14; // SRAV
 - o 32: ALUCtrl o = 2; // ADD
 - o 34: ALUCtrl o = 6; // SUB
 - o 36: ALUCtrl_o = 0; // AND
 - o 37: ALUCtrl o = 1; // OR
 - o 42: ALUCtrl o = 7; // SLT
- Decoder Output Signals (input [4:0] instr_op_i;)
 - RegWrite = 1, if instr_op_i ∈ {0, 35, 8, 9, 15, 13}
 R-type, Load, ADDI, SLTIU, LUI, ORI
 -> nead to write result to some register
 - O ALU_op =

- ALUSrc = 1, if instr_op_i ∈ {35, 43, 8, 9, 15, 13}
 Load, Store, ADDI, SLTIU, LUI, ORI
 -> multiplexer selects [15:0] as the second ALU source
- RegDst = 1, if instr_op_i == 0
 R-type
 -> multiplexer selects [15:11] as the register to write to
- Branch = 1, if instr_op_i \in {4, 5} BEQ, BNE
- Simple_Single_CPU
 - keep_sign (KeepSign) = 1, if inst[31:26] ∈ {9, 13}
 Keep sign (Zero-extend) if op is SLTIU, ORI
 - Assign shamt ([10:6]) as the first ALU source if op is SRA

```
TakeBranch =BEQ -> ZeroBNE -> !Zero
```

Problems Encountered and Solutions

- Errors related to timing (eg. results come after 1 clock cycle later)
 Solution: Change all nonblocking assignments to blocking assignments.
- General debugging difficulties
 Debugging is a pain throughout the implementation.

 Solution: Declare an always block and use \$display to see the contents in the variables during simulation (evaluation).

```
always @(*) begin

$display("%b", inst);

// $display("addr_nxt1 = %d, addr_nxt2 = %d, addr = %d, addr_nxt = %d", addr_nxt1,
addr_nxt2, addr, addr_nxt);

$display("%b", RegWrite);

// $display("%b %b", RegRead1, reg_read1);

$display("%d %d => %d ", reg_data1, reg_data2, res_alu);

end
```

Lesson Learned (If Any)

- Debugging is surprisingly difficult with so many modules in 1 place.
 Next time it's probably wise to test individual components first, but even that would be kind of troublesome.
- Read the samples first to make sure that I truly understand the MIPS operations.